

**HO CHI MINH UNIVERSITY OF TECHNOLOGY**  
**COMPUTER SCIENCE AND ENGINEERING**



Digital Design with the Verilog

CO2010

**Laborary 2**

**Using RTL Design to implement a combinational logic**

**HCMC, 2017**

Objective .....	3
Requirement.....	3
I. The combination circuit using RLT Method .....	3
1. Design Mux 2_to_1 module using “assign”. .....	3
2. RTL Viewer. ....	5
3. Implementation Mux 4_to_1 using Schematic block .....	6
II. Exercise:.....	10

## Objective

- ❖ *Practicing RTL Desing in the combinational circuit (with “assign”).*
- ❖ *How to design circuit by creating a schematic.*
- ❖ *How to check the RTL schematic using Quartus II.*

## Requirement

- ❖ *Submit file code Verilog (.v), file block diagram/schematic (.bdf), and a waveform screen when checking circuit under .zip or .rar with name LAB2\_MSSV.[zip,rar].*

### I. The combination circuit using RLT Method

#### 1. Design Mux 2\_to\_1 module using “assign”.

**Step 1.** Create new project in Quartus II IDE.

**Note:** *FPGA chip is Cyclone IV EP4CGX150DF31C7.!*

**Step 2.** Create new Verilog HDL file.

**Step 3.** Describe Mux 2\_to\_1 module as below code:

```
module mux_2to1 (out, sel, in0, in1);  
    output out;  
    input sel;  
    input in0;  
    input in1;  
  
    assign out = (sel == 1'b0) ? in0 : in1;  
  
endmodule
```


The “assign out = (sel == 1'b0) ? in0 : in1;” means if any input signals such as sel, in0, or in1 changes, the output signal will alter as followed rules:

- If sel == 1'b0, then out = in0.
- If sel == 1'b1, then out = in1.


**Step 4.** Save Verilog filename correctpense with module’s name.

**Step 5.** Set mux\_2to1 as Top level module.

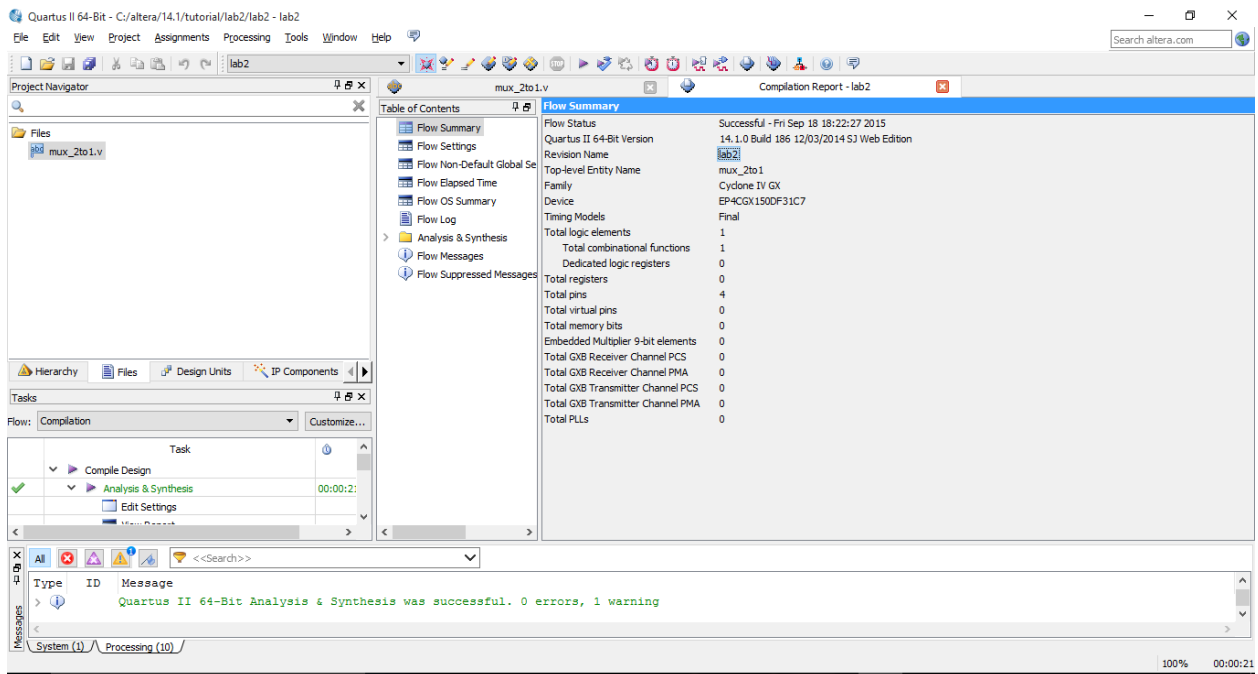**Step 6.** Processing → Start → Start Analysis & Synthesis. If succeed, there is a Flow Summary as the below picture.



**Step 7. Pin assignment for INPUT, OUTPUT signals by choosing .Assignments → Pin Planner. The Pin Planner will appear as the below image.**

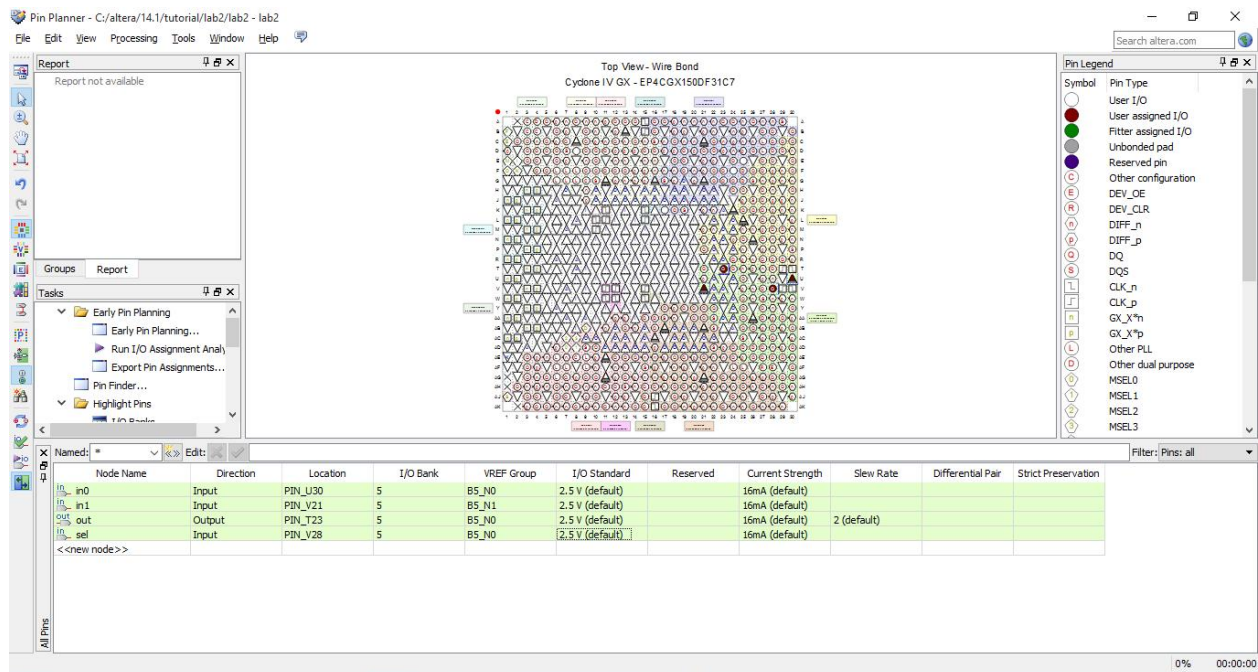

**Figure Error! No text of specified style in document.-2 Pin Planner.**

Assign pins as the Table 2-1:

**Table Error! No text of specified style in document.-1 Pin Assignment.**


Tín hiệu	Loại	Tên	Chân
out	output	LEDR[0]	PIN_T23
sel	input	SWITCH[0]	PIN_V28
in0	input	SWITCH[1]	PIN_U30
in1	input	SWITCH[2]	PIN_V21

**Step 8.** Compile, Install and Check the logic in DE2i-150 board by Processing → Start Compilation (or press Ctrl + L)

## 2. RTL Viewer.

To see RTL view of a module, first, we have to Analysis and Synthesis. Then **Set top level** for the module which needs to see RTL design. And in this lab, it is **mux\_2to1.v**.

Double Click to **RTL viewer** option in **Task** window.

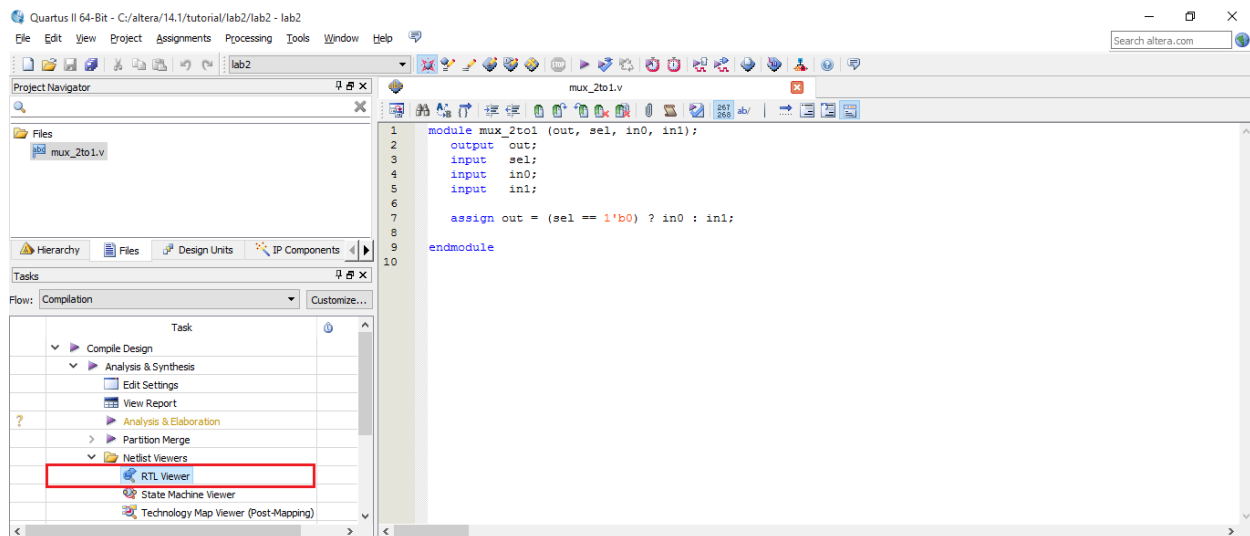

**Figure Error! No text of specified style in document.-3 RTL Viewer Option.**

Then we get the result in RTL Viewer window:

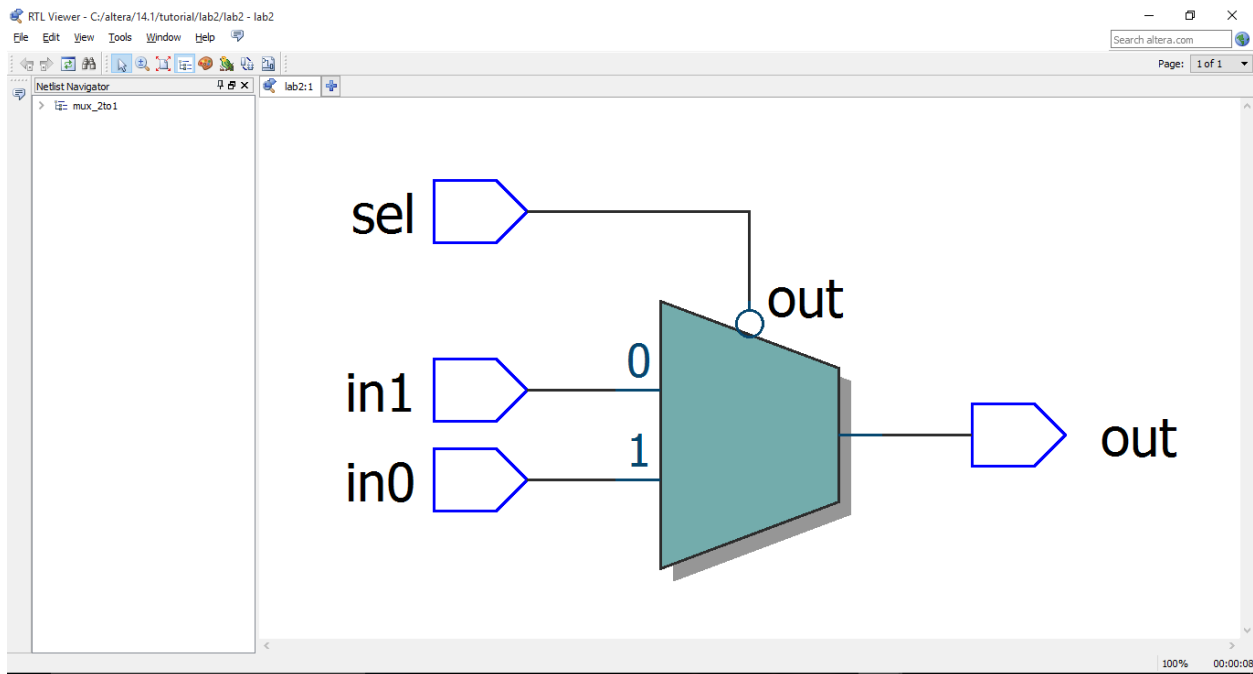


Figure Error! No text of specified style in document.-4 mux 2to1 structure in RTL.

### 3. Implementation Mux 4\_to\_1 using Schematic block

**Step 9.** Create mux 2to1 symbol to use in designing by schematic.

- + In Project Navigator window → choose File tab → next choose mux\_2to1.v file → Create Symbol Files for Current File
- + Or File → Create/Upload → Create Symbol Files for Current File.

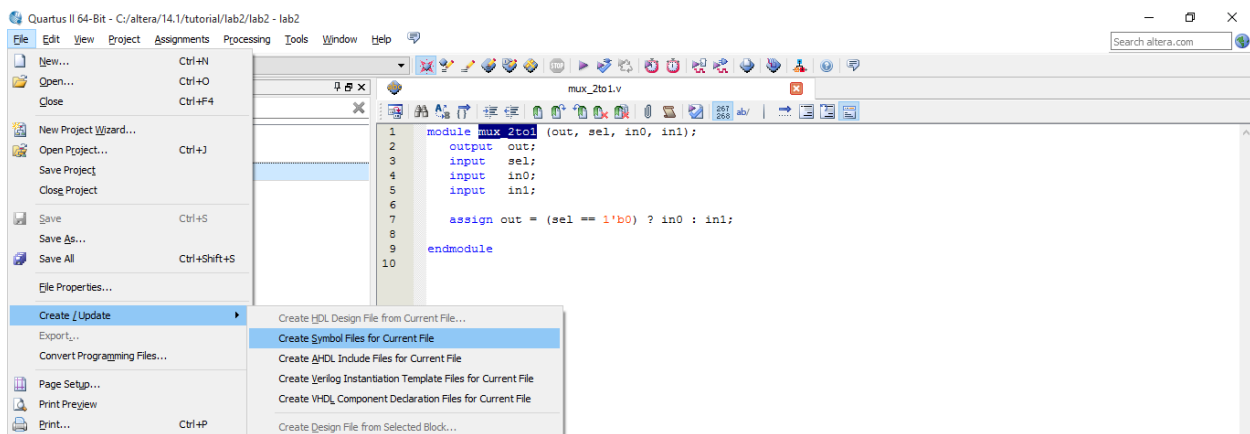

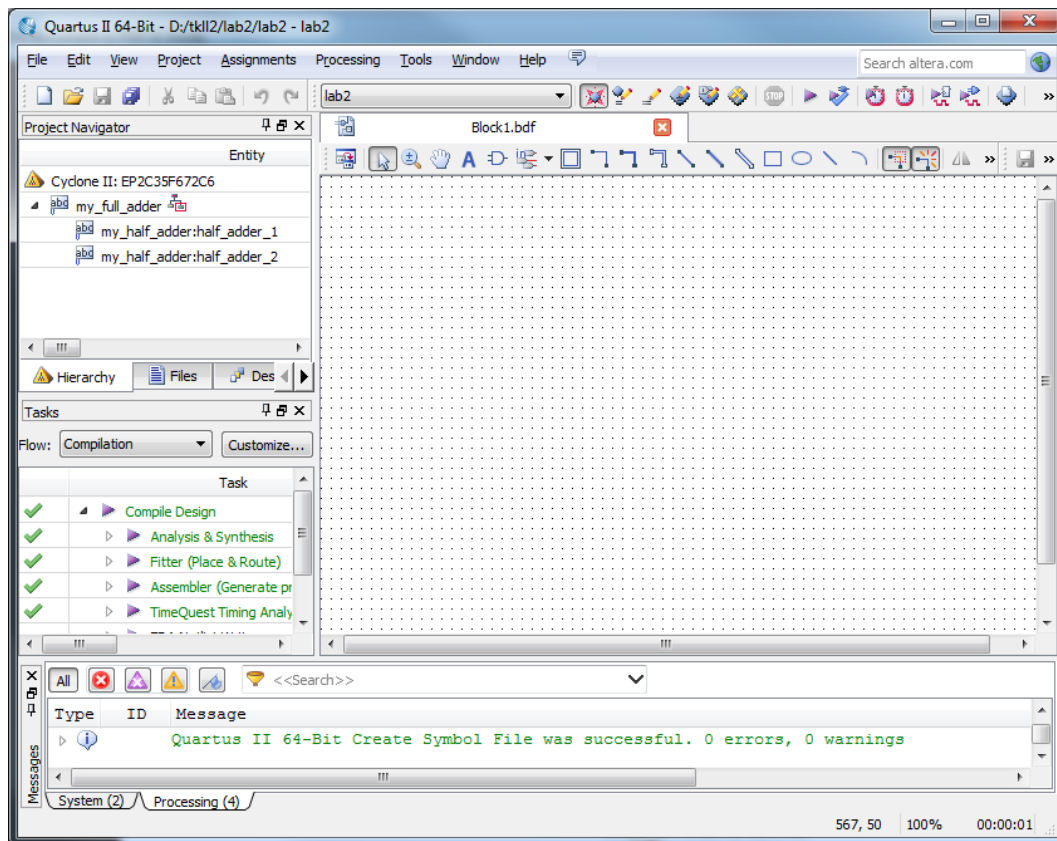


Figure Error! No text of specified style in document.-5 Create symbol for mux\_2to\_1 file.











**Step 10.** Create Schematic file.

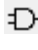
**File** → **New** or  symbol in an accessory bar. Then select **Block Diagram/Schematic File** type and **OK**. The window to design schematic is display as below:




**Figure Error! No text of specified style in document.-6 Schematic Design window.**

**Step 11.** Some tools for designing in the Schematic window.

-  (*Select tool*): select a component in the schematic window.
-  (*Text tool*) : create a text component in the schematic window.
-  (*Symbol tool*): Logic components to design such as logic gate, or megafunction.
-  (pin tool): create input, output, and bidir pin.
-  (*Block tool*): create a function block which makes the design hierarchy.
-  (*orthogonal node tool*): connector
-  (*orthogonal bus tool*): bus connector
-  (*Zoom tool*): zoom in and zoom out.
-  (*Full Screen*): choose to work in Full Screen option or not.
-  (*Find*): find a component.

**Step 12.** Next choose the  (Symbol tool)


In the Libraries window, choose **Project** -> mux\_2to1 symbol -> OK.

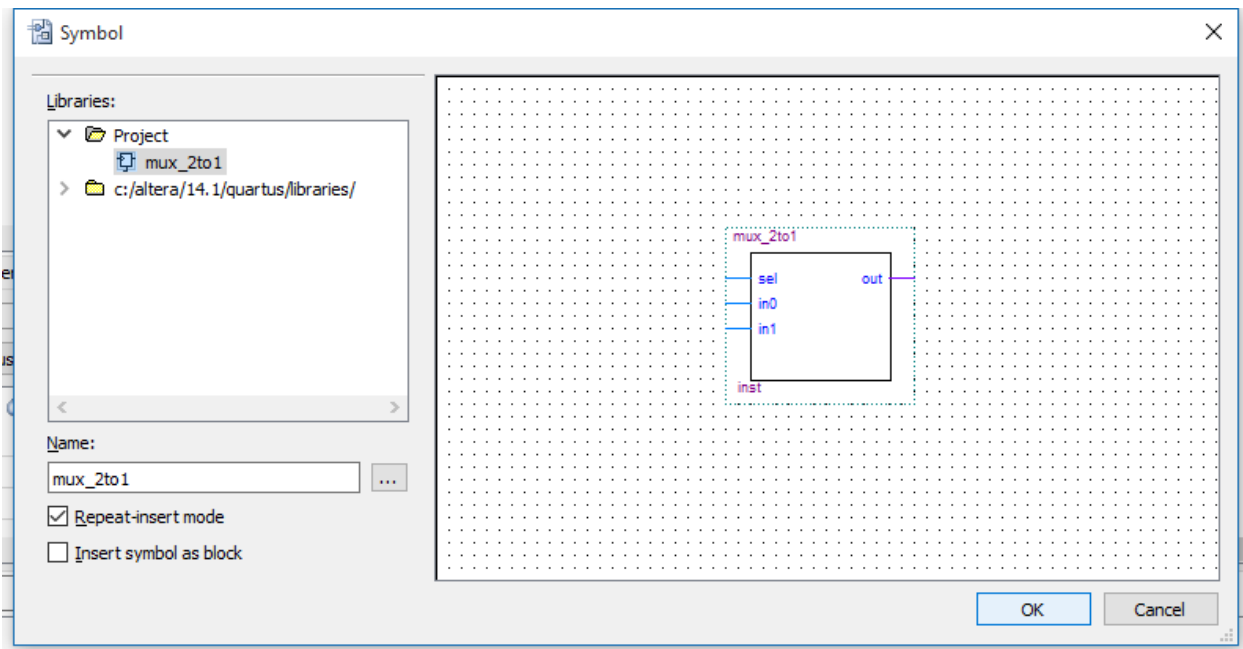


**Figure Error! No text of specified style in document.-7 Symbol window.**

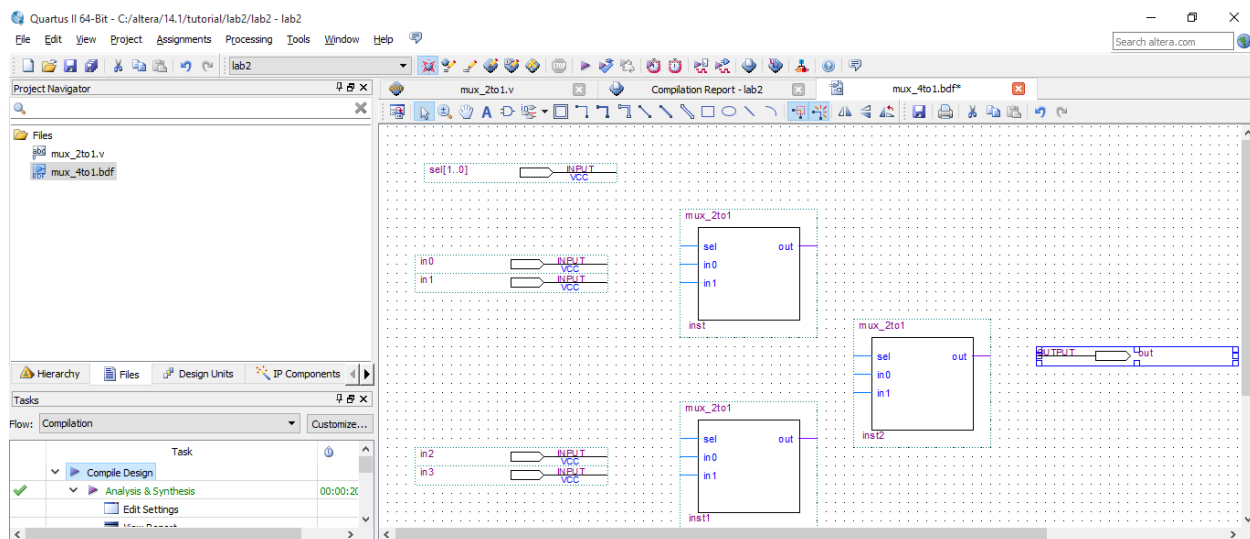**Step 13.** Add two more mux\_2to1 symbol as below

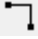

**Step 14.** Add input, output pin.


Choose  (pin tool), add pins, and change name by double click on the pin. The result is as below:



**Figure Error! No text of specified style in document.-8 Add input and output pin for the design.**




**Step 15.** Connect the pin by click  (orthogonal node tool) or the bus by click  (orthogonal bus tool), then drag the mouse from a source location to destination location.

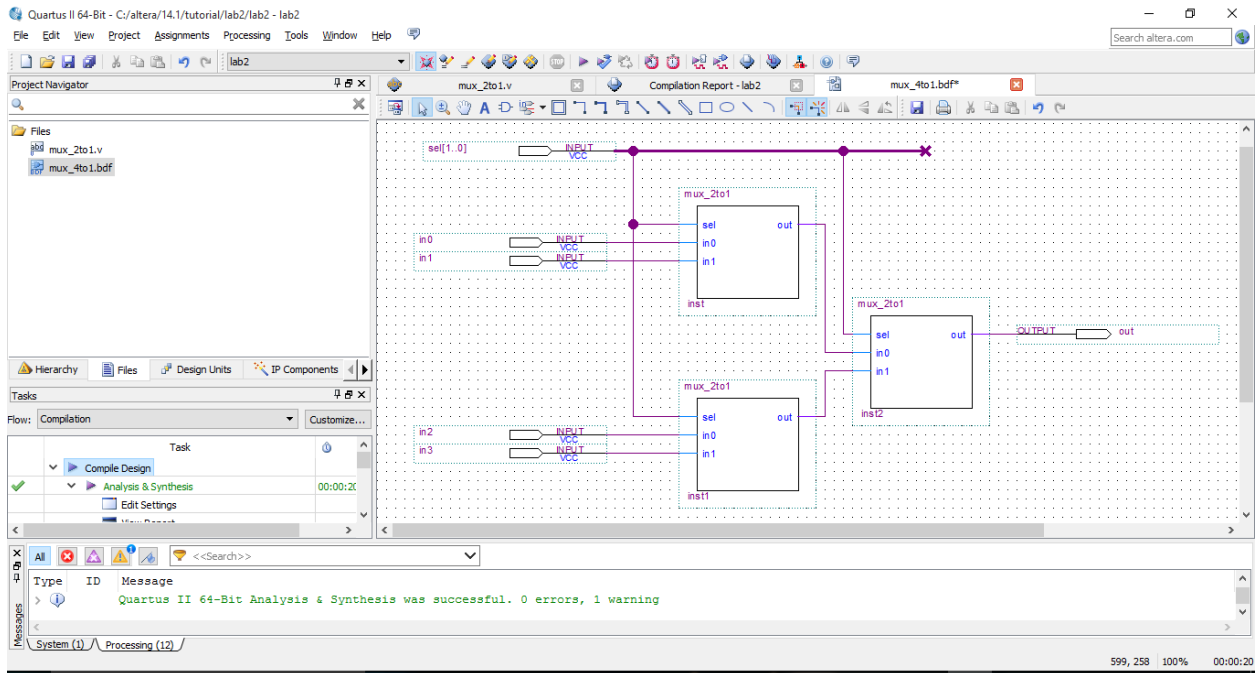

**Figure Error! No text of specified style in document.-9 After connecting pin and bus.**

**Step 16.** Save schematic design file in .bdf format.

**Step 17.** Set Top level module

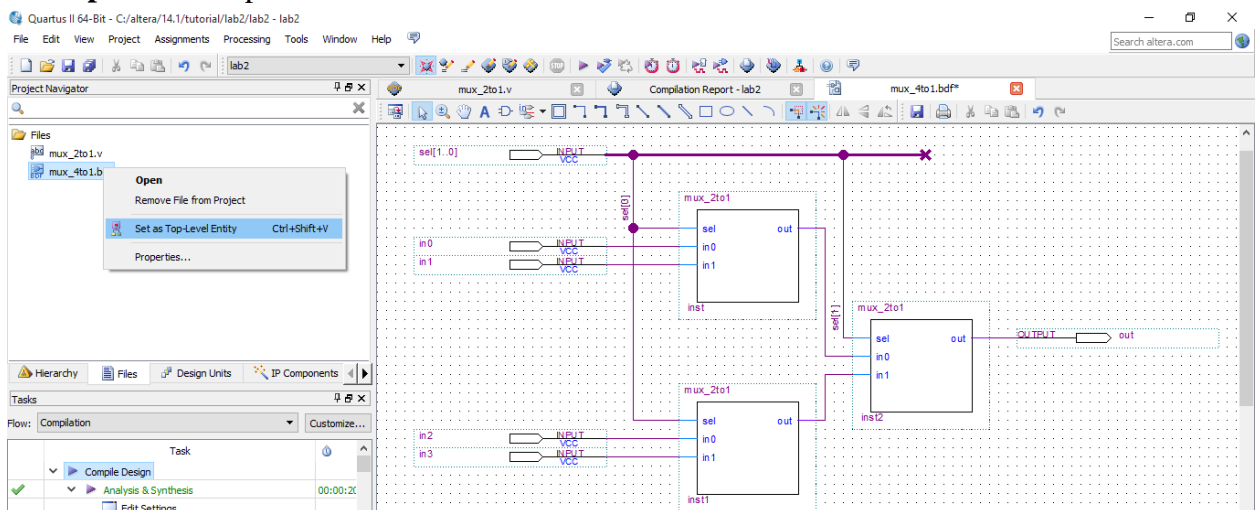

**Figure Error! No text of specified style in document.-10 Set Top level module**

**Step 18.** The Analysis & Synthesis.


**Step 19.** Pin Assignment. Note: delete the old pin from the previous design for mux\_2to1 module.

Assign pin as the below table:

Signal	Type	Name	Pin
out	output	LEDR[0]	PIN_T23
sel[0]	input	SWITCH[0]	PIN_V28
sel[1]	input	SWITCH[1]	PIN_V21
in0	input	SWITCH[2]	PIN_C2
in1	input	SWITCH[3]	PIN_AB30
in2	input	SWITCH[4]	PIN_U21
in3	input	SWITCH[5]	PIN_U30

**Table Error! No text of specified style in document.-2 Pin table for mux\_4to2 module.**

**Step 20.** Compile file to get the result as follow:

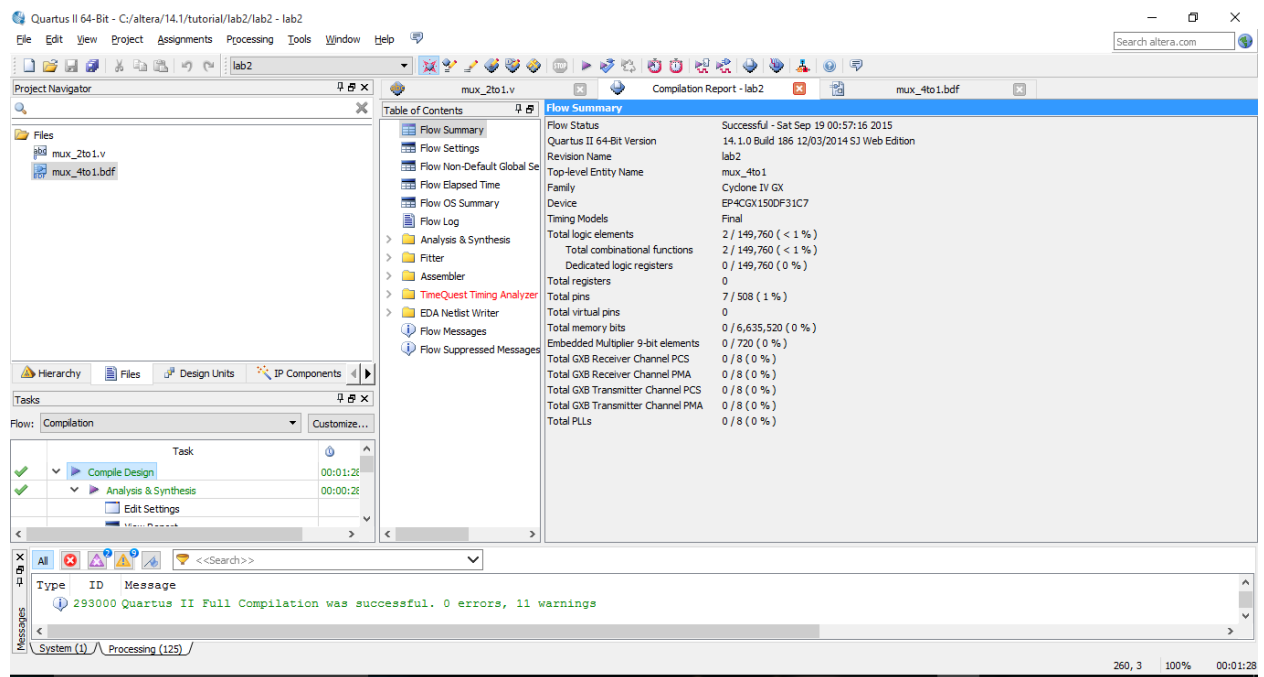


**Figure Error! No text of specified style in document.-11 Compilation result.**

**Step 21.** Install and test on DE2i-150 board.

## II. Exercise:

- [4 points] Design a BCD Decoder to 7-segment LED with the module name is BCD\_2\_Led7seg (led7seg, enable, BCDin).Detail:
  - If enable = 0, then the system is disabled with 7-segment LEDs turn off.
  - If enable = 0, then decode a BCD number from 4-bits to 7-segment LEDs.
  - Note: 7-segment LEDs active HIGH.

Requirment:

 

- a) Code using the RTL method (with assign) (2 points).
  - b) Create file testbench to test the module (2 points).
  - c) Take picture of RTL schematic (is a must for the report).
2. [8 points] Design a comparison circuit with 2 input [3:0] A, [3:0] B and 1 output [2:0] result. Detail:
  - If  $A > B$  then result [0] = 1, otherwise result [0] = 0.
  - If  $A = B$  then result [1] = 1, otherwise result [1] = 0.
  - If  $A < B$  then result [2] = 1, otherwise result [2] = 0.

The module's name is `comparison (result, A, B)`. Input A, B are assigned to 8 SWITCHs, and output result is connected to 3 LEDRs.

  - a) Code using the RTL method (with assign) (2 points).
  - b) Create file testbench to test the module (2 points).
  - c) Take picture of RTL schematic (is a must for the report).
  - d) Design with Schematic: Display input A to HEX6 (a 7-seg LED), and input B to HEX4, then output signal to LEDR (2 points).
  - e) Extend: Compare two 5-bits number and output to 7-segment LED using RLT design, input A is out to HEX6 and HEX7, input B is out to HEX4 and HEX5. The result is out to HEX0 with the rule: if  $A > B$  then result = 1,  $A = B$  then result = 0,  $A < B$  then result = 2 (2 points).